

# EEC 221 - Circuits2 cheat sheet<sup>1</sup>

## Transfer function

$$\mathbf{H}(\omega) = \frac{\mathbf{Y}(\omega)}{\mathbf{X}(\omega)}$$

$$\text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$$

$$\text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\text{Transfer impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\text{Transfer admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

$$\text{For RC circuit: } \omega_0 = \frac{1}{RC}$$

$$\text{For RL circuit: } \omega_0 = \frac{R}{L}$$

## Resonance

### Series resonance

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

at resonance:

$$Z = R \quad |I|_{max} = \frac{|V|_{max}}{R} \quad X_L = X_C$$

The average power at RLC circuits:

$$P(\omega) = \frac{1}{2} I^2 R$$

The average power at resonance:

$$P(\omega) = \frac{1}{2} I_{max}^2 R = \frac{1}{2} \frac{V_{max}^2}{R}$$

Half power frequencies:

$$\omega_{1,2} = \mp \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

Bandwidth:

$$B = \omega_2 - \omega_1 = \frac{R}{L}$$

Quality factor:

$$Q = \frac{\text{Peak energy}}{\text{Energy dissipated}} = \frac{\omega_0}{B}$$

When  $Q > 10$  :

$$\omega_1 = \omega_0 - \frac{B}{2}$$

$$\omega_2 = \omega_0 + \frac{B}{2}$$

### Parallel resonance

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

at resonance:

$$Z = R \quad |I|_{max} = \frac{|V|_{max}}{R} \quad X_L = X_C$$

The average power at RLC circuits:

$$P(\omega) = \frac{1}{2} I^2 R$$

The average power at resonance:

$$P(\omega) = \frac{1}{2} I_{max}^2 R = \frac{1}{2} \frac{V_{max}^2}{R}$$

Half power frequencies:

$$\omega_{1,2} = \mp \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

Bandwidth:

$$B = \omega_2 - \omega_1 = \frac{1}{RC}$$

Quality factor:

$$Q = \frac{\text{Peak energy}}{\text{Energy dissipated}} = \frac{\omega_0}{B}$$

When  $Q > 10$  :

$$\omega_1 = \omega_0 - \frac{B}{2}$$



$$\omega_2 = \omega_0 + \frac{B}{2}$$

## Magnetically Coupled Circuits


M (Mutual inductance):

$$M = K\sqrt{L_1 L_2} \quad (\text{k: coupling coefficient})$$

Dot convention:

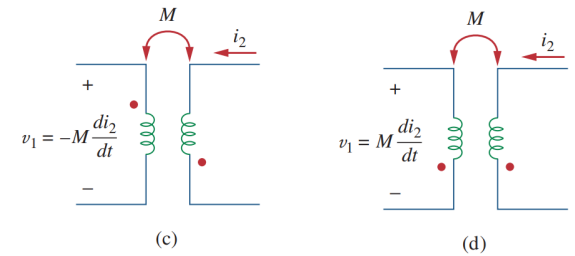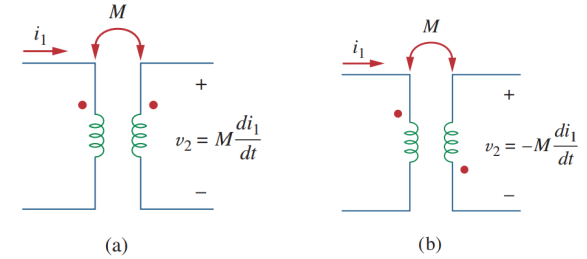


Dependent source representation:

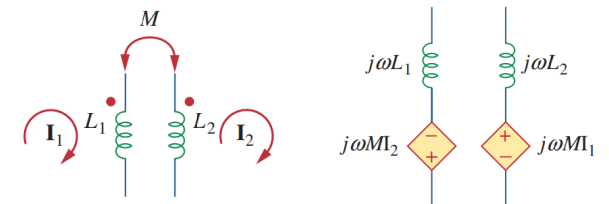

Series-aiding connection:


$$l_{eq} = L_1 + L_2 + 2M$$

<sup>1</sup>Taha Ahmed

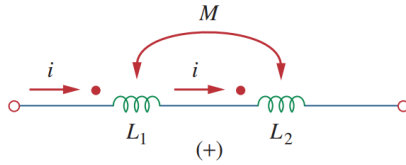

Series-aiding connection:

$$l_{eq} = L_1 + L_2 - 2M$$

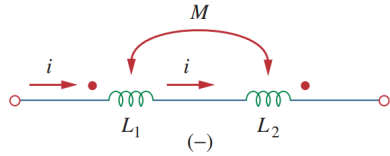

Energy stored:

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

(two currents enter the dots or leave)

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - M I_1 I_2$$


(one enters, one leaves)

Power dissipated in a resistor:


$$P = |I_{RMS}|^2 R \quad (I_{RMS} = \frac{I_{peak}}{\sqrt{2}})$$

$$P = \frac{1}{2} |I_{peak}|^2 R$$

T model:

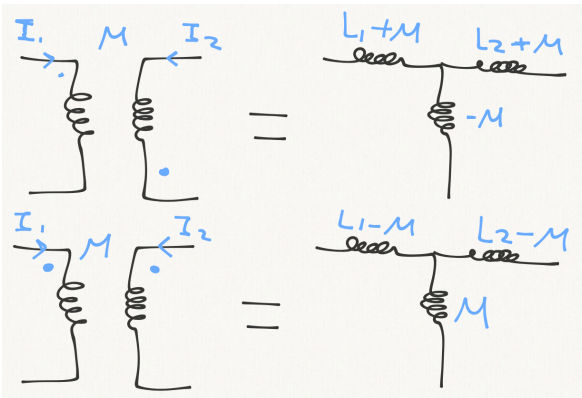

$\pi$  model:

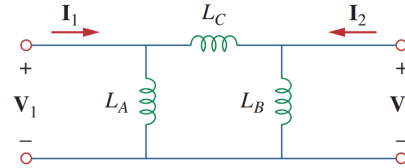


$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M} \quad L_B = \frac{L_1 L_2 - M^2}{L_1 - M}$$

$$L_C = \frac{L_1 L_2 - M^2}{M}$$

## Transformer

Linear transformer  $0 < k < 1$

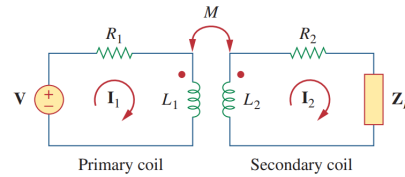

$$Z_{in} = R_1 + j\omega L_1 + \underbrace{\frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}}_{\text{reflected impedance}} = \frac{V}{I_1}$$

$$Z_{th} = R_2 + j\omega L_2 + \underbrace{\frac{\omega^2 M^2}{R_1 + j\omega L_1}}_{\text{reflected impedance}}$$

for maximum power transfer:

$$Z_L = Z_{th}^*$$

for maximum power transfer if  $R_L$  is pure resistive:

$$R_L = |Z_{th}|$$

Ideal transformer  $k = 1$

$$n = \frac{N_2}{N_1}$$

$$\frac{V_2}{V_1} = n$$

$$\frac{I_2}{I_1} = \frac{1}{n}$$

(turns ratio)

Referring from secondary to primary:

$$V_1' = \frac{V_2}{n}$$

$$I_1' = n I_2$$

$$Z_1' = \frac{V_2}{n^2}$$

Referring from primary to secondary:

$$V_2' = n V_1$$



$$I_2' = \frac{I_1}{n}$$

$$Z_2' = n^2 Z_1$$

Sign roles:

if both voltages are +ve or -ve relative to the dotted terminals  $\rightarrow$  use  $+n$   
otherwise use  $-n$

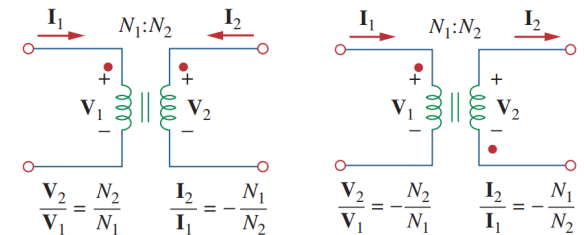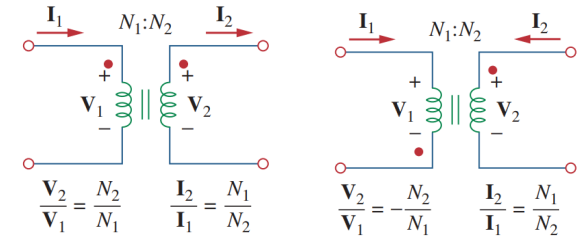if both currents enter or leave the dotted terminals  $\rightarrow$  use  $-n$   
otherwise use  $+n$




Complex power:

$$s_1 = V_1 I_1^*$$

$$s_2 = V_2 I_2^*$$

$$s_1 = s_2$$

## Ideal autotransformer

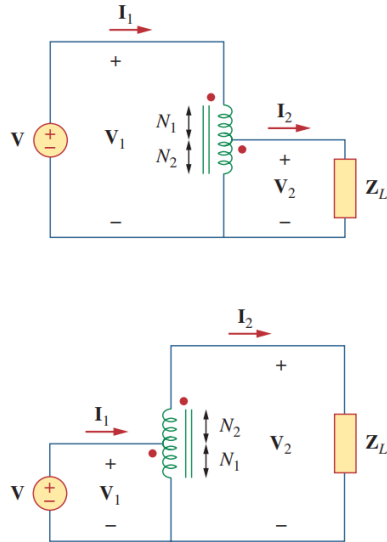

(a) Step-down autotransformer, (b) step-up autotransformer.

Step down autotransformer:

$$\frac{V_1}{V_2} = \frac{N_1 + N_2}{N_2}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1 + N_2}$$

Step up autotransformer:

$$\frac{V_1}{V_2} = \frac{N_1}{N_1 + N_2}$$

$$\frac{I_1}{I_2} = \frac{N_1 + N_2}{N_1}$$

## Two port network

Impedance parameters [Z]

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

for any T network:

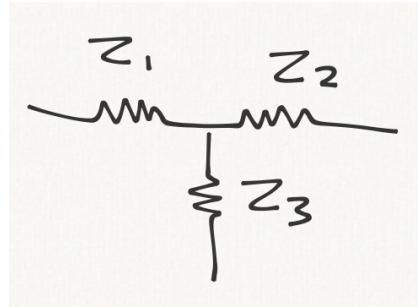

$$Z = \begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix}$$

if  $Z_{11} = Z_{22} \rightarrow$  symmetrical network

if  $Z_{12} = Z_{21}$  and has no dependent sources  $\rightarrow$  reciprocal network

Admittance parameters [y]

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$


$$y_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

for any T network:

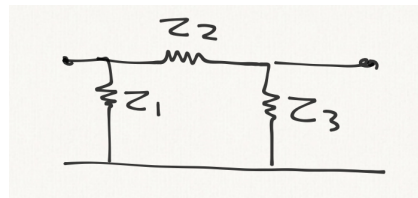

$$y = \begin{bmatrix} \frac{1}{Z_1} + \frac{1}{Z_2} & -\frac{1}{Z_2} \\ -\frac{1}{Z_2} & \frac{1}{Z_2} + \frac{1}{Z_3} \end{bmatrix}$$

note that

$$[Z] = [y]^{-1}$$

remember  $\rightarrow$  Let

$$A = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix}$$

be a full-rank  $2 \times 2$  matrix. Then  $\det A \equiv |A| = a_{11}a_{22} - a_{12}a_{21} \neq 0$  and

$$A^{-1} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix}^{-1} = \frac{1}{|A|} \begin{bmatrix} a_{22} & -a_{12} \\ -a_{21} & a_{11} \end{bmatrix}.$$

Hybrid parameters [h]

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

Inverse Hybrid parameters [g]

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

note that

$$[g] = [h]^{-1}$$

Transmission parameters [T]

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_2}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

**Inverse transmission parameters [t]**

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

$$\begin{aligned} V_2 &= aV_1 - bI_1 \\ I_2 &= cV_1 - dI_1 \end{aligned}$$

$$\begin{aligned} a &= \left. \frac{V_2}{V_1} \right|_{I_1=0} & b &= \left. \frac{-V_2}{I_1} \right|_{V_1=0} \\ c &= \left. \frac{I_2}{V_1} \right|_{I_1=0} & d &= \left. \frac{-I_2}{I_1} \right|_{V_2=0} \end{aligned}$$

note that

$$[t] \neq [T]^{-1}$$

Network is reciprocal if  $ad - bc = 1$

**Interconnection of networks**

**Series-series**

$$Z_T = Z_1 + Z_2$$

**Parallel-parallel**

$$y_T = y_1 + y_2$$

**Series-parallel**

$$h_T = h_1 + h_2$$

**Parallel-series**

$$g_T = g_1 + g_2$$

**Cascaded**

$$[T_T] = [T_1] [T_2] \qquad \text{(matrix multiplication)}$$